

BTECH
(SEM III) THEORY EXAMINATION 2021-22
NETWORK ANALYSIS AND SYNTHESIS

Time: 3 Hours

Total Marks: 100

Note: 1. Attempt all Sections. If require any missing data; then choose suitably.

SECTION A

1. Attempt all questions in brief.

2 x 10 = 20

- a. Illustrate the admittance parameter of a two-port network.
- b. Describe the band stop filter with suitable example.
- c. Demonstrate time scaling property of Laplace transform.
- d. Describe the singularity function with suitable example.
- e. Demonstrate time convolution property of Fourier transform.
- f. Illustrate the drawback of Fourier Transform and how this drawback can be removed by using Laplace transform.
- g. Describe and state Thevenin's theorem with suitable example.
- h. Describe the following terms for a network: Graph, Tree, Co-Tree, and Twig.
- i. Use source transformation to solve in the circuit shown in figure 1.

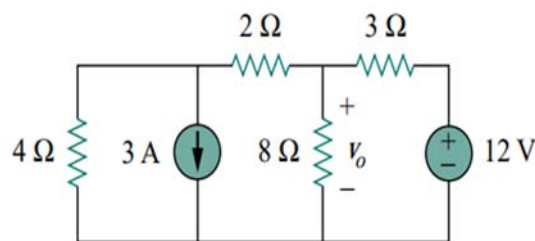


Figure 1

- j. When the voltage across a resistor is 120 V, the current through it is 2.5 mA. Calculate its conductance.

SECTION B

2. Attempt any three of the following:

10 x 3 = 30

- a. Identify the node voltages in the circuit shown in figure 2.

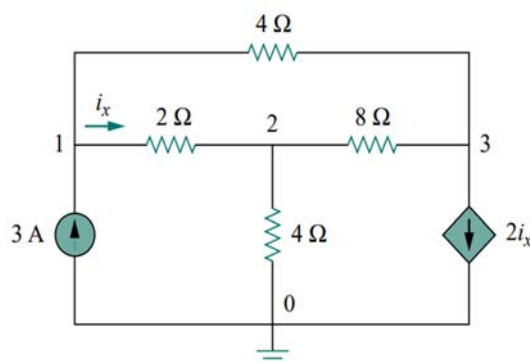


Figure 2

BTECH
(SEM III) THEORY EXAMINATION 2021-22
NETWORK ANALYSIS AND SYNTHESIS

- b. Find i_o in the circuit shown in the figure 3 using superposition.

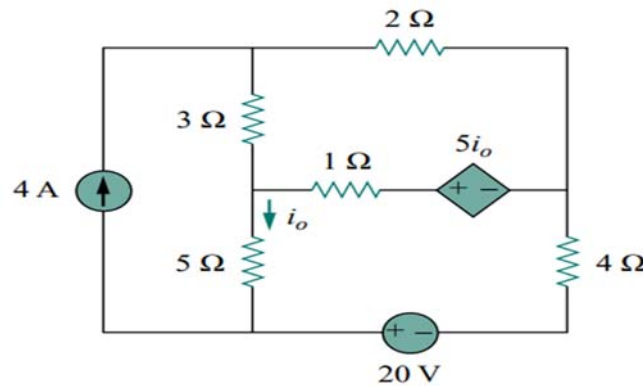


Figure 3

- c. Calculate the Fourier Transform for the signal
$$x(t) = t^2 e^{-at} u(t)$$
- d. Find the Laplace transform for the given signal.
$$x(t) = \left(\frac{1 - e^{-t}}{t} \right) u(t)$$
- e. Illustrate the low pass filter. Derive the expression for transfer function of a low pass filter and plot the curve.

SECTION C

3. Attempt any one part of the following:

10 x 1 = 10

- (a) Describe the following terms with example.
- i. Junction Point
 - ii. Node
 - iii. Branch
 - iv. Active and Passive Network
 - v. Linear and Non-Linear Network

- (b) Calculate the mesh currents i_1 and i_2 in the circuit shown in figure 4.


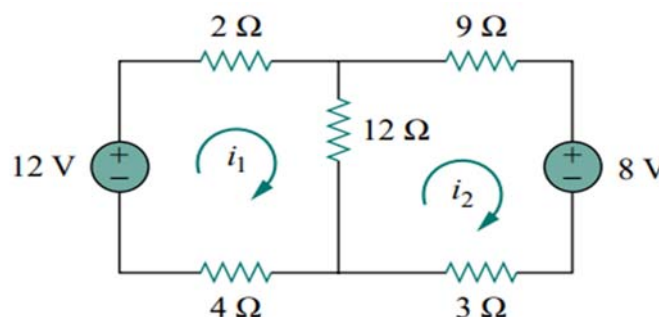


Figure 4

 

- (b) Illustrate the high pass filter. Derive the expression for transfer function of a high pass filter and plot the curve.