



PAPER ID-411535

Printed Page: 1 of 3
Subject Code: KOE037

Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

BTECH
(SEM III) THEORY EXAMINATION 2021-22
ANALOG ELECTRONICS

Time: 3 Hours**Total Marks: 100****Note:** Attempt all Sections. If you require any missing data, then choose suitably.**SECTION A****1. Attempt all questions in brief.****2*10 = 20**

Qno	Questions	CO
(a)	Write name of any four diode circuits and draw low frequency hybrid- π model of BJT.	1
(b)	What is objective of different biasing schemes for BJT and FET amplifier?	1
(c)	Define different parameters used in high frequency hybrid- π model.	2
(d)	What is effect of negative feedback on gain and bandwidth?	2
(e)	In an RC phase shift oscillator, $R = 200\text{ K}\Omega$ and $C = 200\text{pF}$. Find the frequency of BJT –based oscillator.	3
(f)	Explain Barkhausen criterion.	3
(g)	Differentiate between CMRR and ICMR for a differential amplifier.	4
(h)	Determine the range of differential-mode operation of MOS differential Pair of overdrive voltage (V_{ov}) is 1V.	4
(i)	Draw the circuit of precision half wave rectifier and its ideal transfer characteristic.	5
(j)	What are the limitations of an ideal integrator?	5

SECTION B**2. Attempt any three of the following:****10*3 = 30**


Qno	Questions	CO
(a)	Draw the small signal AC equivalent circuit of a Common Drain FET amplifier. Derive the expression for voltage gain, input impedance and output impedance.	1
(b)	Why class AB power amplifiers are preferred over Class B operations? A transformer-coupled class A power amplifier supplies to an 80Ω load connected across the secondary of a step-down transformer having a turn-ratio 5:1. Determine the maximum power output for a zero signal collector of 120 mA.	2
(c)	Draw the neat circuit diagram of RC phase shift oscillator and derive its frequency of oscillations.	3
(d)	Discuss the basic topology of current mirror and its variants with V-I characteristics.	4
(e)	Sketch the three-input inverting summing circuit and derive an expression for the output voltage. Find out the voltages V_2 and V_3 of the given network.	5



Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

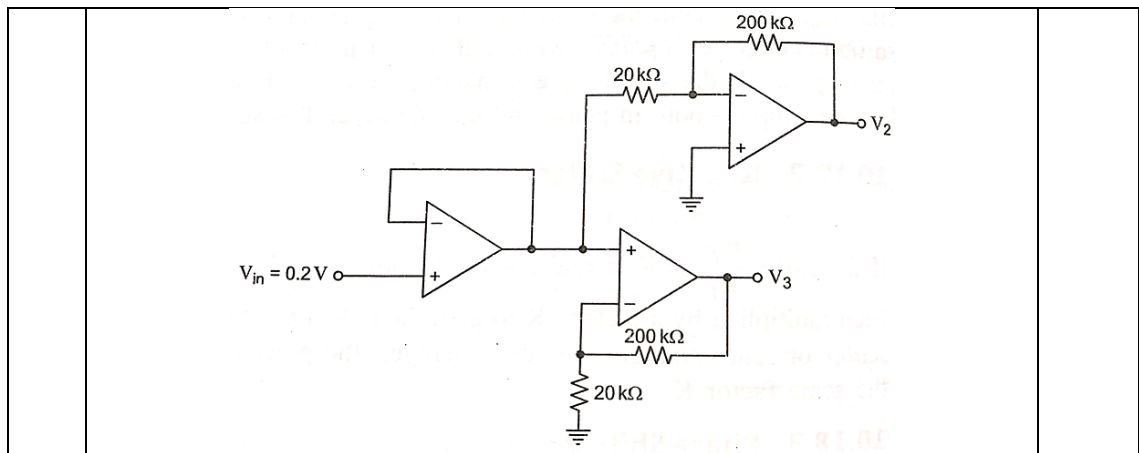BTECH
(SEM III) THEORY EXAMINATION 2021-22
ANALOG ELECTRONICS



SECTION C

3. Attempt any *one* part of the following: 10*1 = 10

Qno	Questions	CO
(a)	What is the significance of stability factor in transistor operation? A voltage divider circuit has $R_1 = 39\text{ K}\Omega$, $R_2 = 82\text{ K}\Omega$, $R_C = 3.3\text{ K}\Omega$, $R_E = 1\text{ K}\Omega$ and $V_{CC} = 18\text{ V}$. The silicon transistor used has $\beta = 120$. Find Q-point and stability factor.	1
(b)	Why does gain of amplifier falls at low and high frequencies? Specify different schemes of coupling in multistage amplifiers. Compare their merits and demerits.	1

4. Attempt any *one* part of the following: 10 *1 = 10

Qno	Questions	CO
(a)	Find the midband gain and the upper 3-db frequency of the common-emitter amplifier shown in given figure for the following case: $V_{CC} = V_{EE} = 10\text{ V}$, $I = 1\text{ mA}$, $R_B = 100\text{ K}\Omega$, $R_C = 8\text{ K}\Omega$, $R_{sig} = 5\text{ K}\Omega$, $R_L = 5\text{ K}\Omega$, $\beta_0 = 100$, $V_A = 100\text{ V}$, $C_\mu = 1\text{ pF}$, $f_T = 800\text{ MHz}$ and $r_x = 50\Omega$.	2
(b)	Explain the block diagram of a feedback amplifier. Draw the block diagram of voltage series feedback amplifier and find the effect of feedback on input and output impedances.	2



Roll No:


--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

BTECH
(SEM III) THEORY EXAMINATION 2021-22
ANALOG ELECTRONICS

5. Attempt any *one* part of the following: 10*1 = 10

Qno	Questions	CO
(a)	Draw the circuit of Wien-bridge oscillator and discuss its basic principle of operation. Also determine frequency of oscillation.	3
(b)	With a neat circuit diagram, explain the operation of Colpitts oscillator. Derive the expression for frequency of oscillation and the minimum gain for sustained oscillations.	3

6. Attempt any *one* part of the following: 10*1 = 10

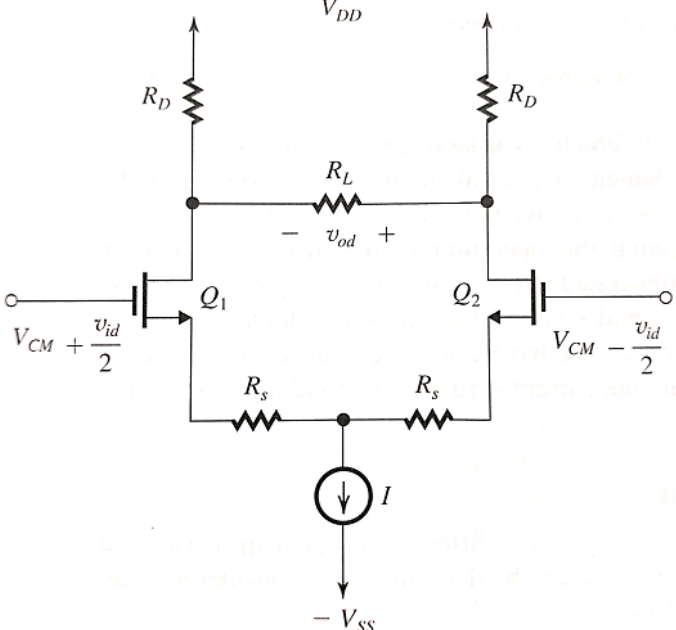Qno	Questions	CO
(a)	Write short notes on any two of the following: (i) Minimum sustainable voltage (V_{ON}) (ii) Maximum usable load (iii) Differential gain and Common mode gain	4
(b)	Give the differential half-circuit of the differential amplifier shown in given figure. Assume that Q_1 and Q_2 are perfectly matched. Neglecting r_o , determine the differential voltage gain. 	4

7. Attempt any *one* part of the following: 10*1 = 10

Qno	Questions	CO
(a)	Explain how a Schmitt Trigger circuit works with a neat diagram. Design an Schmitt trigger with $V_{UT} = 2V$, $V_{LT} = -1V$. Assume $\pm V_{sat} = \pm 13V$	5
(b)	How is order of filter decided? Design a wide band pass filter to meet the following specifications: $f_1 = 5kHz$, $f_2 = 15kHz$ and Pass band gain=2.	5