



Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

B TECH
(SEM-III) THEORY EXAMINATION 2020-21
NETWORK ANALYSIS AND SYNTHESIS

Time: 3 Hours



Total Marks: 100

Note: 1. Attempt all Sections. If require any missing data; then choose suitably.

SECTION A

1. Attempt all questions in brief.


2 x 10 = 20

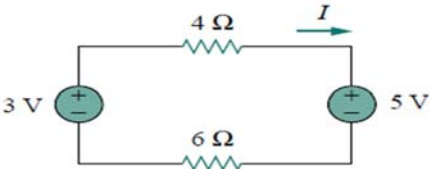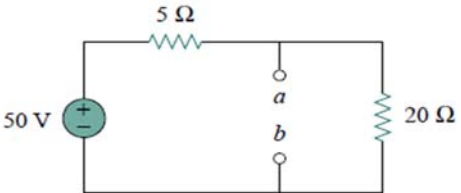Q no.	Question	Marks	CO
a.	Describe the following terms: Tree, Co-Tree, Twig and link.	2	1
b.	Find the current I in the circuit shown in the Figure 1. <div style="text-align: center;">  <p>Figure 1</p> </div>	2	1
c.	Describe and state Superposition theorem with suitable example.	2	2
d.	Find Thevenin voltage across terminals a and b of the circuit shown in the Figure 2. <div style="text-align: center;">  <p>Figure 2</p> </div>	2	2
e.	Illustrate why we use Fourier Transform and what is the drawback of Fourier Transform.	2	3
f.	Demonstrate time reversal property of Fourier transform.	2	3
g.	Describe the Singularity function with suitable example.	2	4
h.	Demonstrate time shifting property of Laplace transform.	2	4
i.	Describe the Band pass filter with suitable example.	2	5
j.	Illustrate the Impedance parameter of a two-port network.	2	5

SECTION B

2. Attempt any three of the following:




10 x 3 = 30

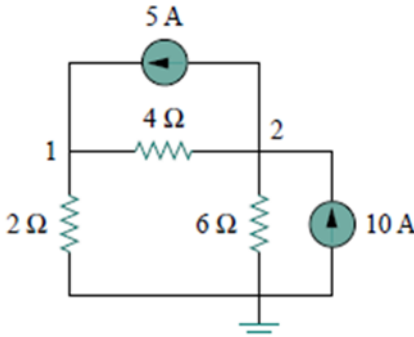Q no.	Question	Marks	CO
a.	Identify the node voltages in the circuit shown in Figure 3. <div style="text-align: center;">  <p>Figure 3</p> </div>	10	1




Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

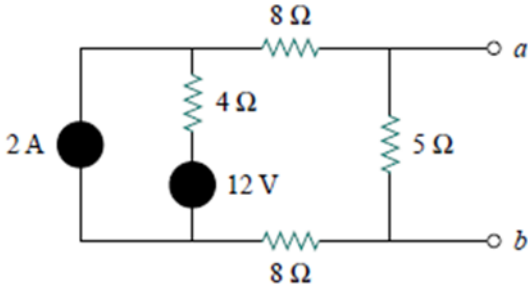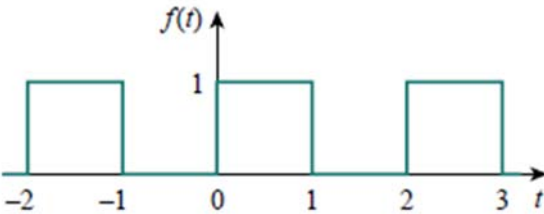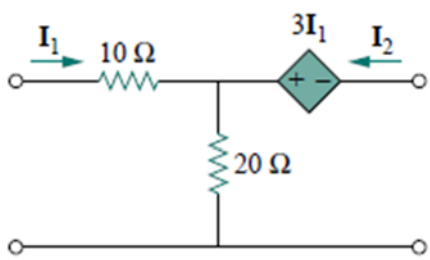b.	Find the Norton equivalent circuit of the circuit in Figure 4.	10	2
 <p style="text-align: center;">Figure 4</p>			
c.	Describe the Fourier series of the waveform shown in Figure 5.	10	3
 <p style="text-align: center;">Figure 5</p>			
d.	Find the Laplace transform for the given signal. $x(t) = e^{at}u(t) * e^{at}u(t)$ where * represents the time convolution.	10	4
e.	Find the transmission parameters for the two-port network in Figure 6.	10	5
 <p style="text-align: center;">Figure 6</p>			

SECTION C



3. Attempt any one part of the following:

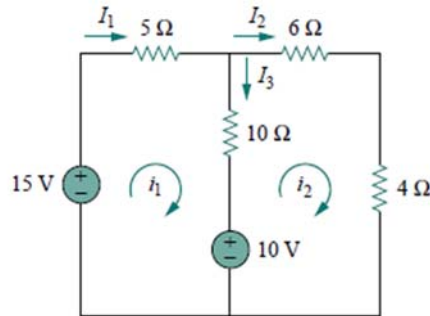a.	For the circuit in Figure 7, find the branch currents I_1 , I_2 , and I_3 using mesh analysis.	10	1
 <p style="text-align: center;">Figure 7</p>			
b.	Describe the following terms with example. i. Junction Point	10	1

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

	ii. Node		
	iii. Branch		
	iv. Active and Passive Network		
	v. Linear and Non-Linear Network		

4. Attempt any one part of the following:

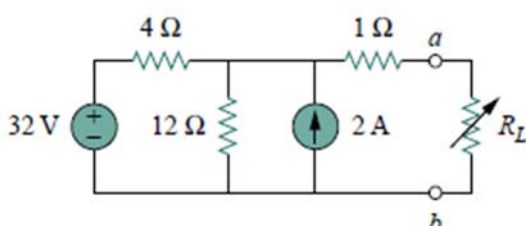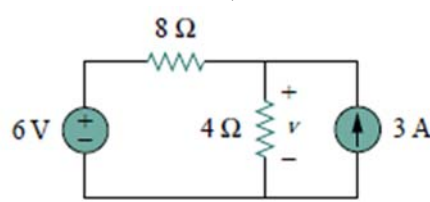a.	Find the Thevenin equivalent circuit of the circuit shown in Figure 8, to the left of the terminals $a-b$.	10	2
 <p style="text-align: center;">Figure 8</p>			
b.	Use the superposition theorem to find v in the circuit in Figure 9.	10	2
 <p style="text-align: center;">Figure 9</p>			

5. Attempt any one part of the following:

a.	Find out the Fourier Transform for the Gate function (Rectangular pulse). Also draw the magnitude spectrum of the output.	10	3
b.	Demonstrate time convolution and time scaling property of Fourier transform. Also mention their significance.	10	3

6. Attempt any one part of the following:

a.	Find the Laplace transform for the given signal and calculate the ROC.	10	4
$x(t) = t^2 e^{-3t} u(t)$			
b.	Derive the expression for source free RLC circuit and discuss all three cases: Overdamped response, Underdamped response, and critical damped response.	10	4

7. Attempt any one part of the following:

a.	Illustrate the high pass filter. Derive the expression for transfer function of a high pass filter and plot the curve.	10	5
b.	Obtain the relation for Y and H parameters of a two-port network, when Z-parameter is given.	10	5