

Roll No:

BTECH
(SEM IV) THEORY EXAMINATION 2021-22
DIGITAL ELECTRONICS

Time: 3 Hours

Total Marks: 100

Note: 1. Attempt all Sections. If require any missing data, then choose suitably.

SECTION A

1. Attempt all questions in brief.

2 * 10 = 20

Q no	Question	CO
a	Identify the value of x in the expression $(561A)_{16} = (x)_8$.	1
b	Perform the subtraction $(101101-100110)_2$ using 2's complement method.	1
c	Compare serial adder and parallel adder	2
d	What is difference between combinational and sequential circuits.	2
e	The content of 4 bit register is initially 1101. The register is sifted six time to right with the serial input being 101101. What is the content of the register after sixth shift?	3
f	If in an edge triggered JK flip flop, $J=1$, $K=1$ and $Q=1$, when the clock pulse goes HIGH, what would be the next state of Q .	3
g	Define critical race and non-critical race conditions.	4
h	Differentiate synchronous and asynchronous sequential circuits.	4
i	Write the advantage and disadvantages of TTL and CMOS logic family	5
j	Explain fan-in and fan-out in logic families.	5

SECTION B

2. Attempt any three of the following:

10*3 = 30

Q no	Question	CO
a	Simplify the following Boolean function using K-map and also draw the simplified logic circuit using basic logic gates $f(A,B,C,D) = \sum m(0,1,5,6,12,13,14) + d(2,4)$	1
b	Implement the function $Y(A,B,C,D) = \sum m(0,1,2,5,8,13,14)$ using 8:1 multiplexer. Consider A, B, C as the select lines.	2
c	Differentiate between synchronous and asynchronous counters. Design a 2 bit synchronous UP counter	3
d	An asynchronous sequential circuit with two excitation function with two feedback loop is given as $Y_1 = xy_1 + \bar{x}y_2$; $Y_2 = xy_1 + \bar{x}y_2$ (i) Draw the logic diagram of the circuit. (ii) Derive the transition table & obtain the flow table	4
e	Differentiate RAM and ROM. Explain various types of ROM.	5

SECTION C

3. Attempt any one part of the following:

10*1 = 10

Q no	Question	CO
a	Explain Error detecting and Error correcting codes. A seven-bit Hamming code coming out of a transmission line is 1000010. What was the original code transmitted? Consider the even parity check.	1
b	Express the design of EX-OR gate with the help of (i) NAND gates only and (ii) NOR gates only	1

Roll No:-

BTECH
(SEM IV) THEORY EXAMINATION 2021-22
DIGITAL ELECTRONICS

4. Attempt any one part of the following:

10*1 = 10

Q no	Question	CO
a.	Explain the design of a Full adder, with its truth table and Boolean expression.	2
b.	Design a Binary Code to Gray code Converter, Also show its truth table, Boolean expression and logic diagram	2


5. Attempt any one part of the following:

10*1 = 10

Q no.	Question	CO
a.	Discuss the Race around condition of JK flip flop. How JK flip-flop can be used as T flip-flop, Explain the design procedure	3
b.	Analyze RS flip -flop. using NAND-NAND logic and obtain its characteristic equation and excitation table. Explain how will you convert it in D Flip-flop.	3

6. Attempt any one part of the following:

10*1 = 10

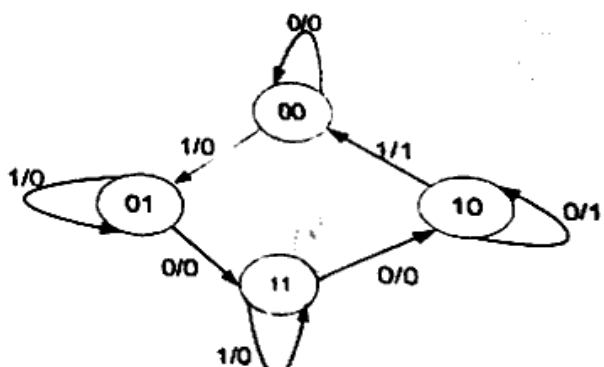Q no	Question	CO															
a.	<p>Implement the circuit defined by the following transition table with a NOR SR Latch. Also show the implementation with NAND SR latch</p> <p style="text-align: center;">$A \times 2$</p> <table border="1" style="margin-left: auto; margin-right: auto;"> <tr> <td></td> <td>00</td> <td>01</td> <td>11</td> <td>10</td> </tr> <tr> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> <td>1</td> <td>1</td> </tr> </table>		00	01	11	10	0	0	0	0	1	1	0	0	1	1	4
	00	01	11	10													
0	0	0	0	1													
1	0	0	1	1													
b.	<p>Write the design procedure for clocked sequential circuits and implement the following state diagram.</p> 	4															

7. Attempt any one part of the following:

10*1 = 10

Q no.	Question	CO
a.	Explain PLA and PAL. Implement the given Boolean function with a PLA. $Y_1(A,B,C) = \sum m(4,5,7); \quad Y_2(A,B,C) = \sum m(3,5,7)$	5
b.	Construct the following logic gates from NMOS and PMOS logic Families (i) NAND (ii) NOR	5