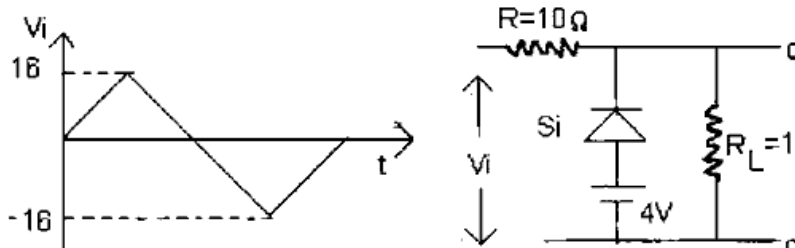





## 4. Attempt any one part of the following:

1 x 10 = 10

| Q no. | Question   | Marks | CO  |
|-------|--|-------|-----|
| a.    | <p>(i) In a full wave rectifier, the input is from 30-0-30V transformer. The load and diode forward resistances are <math>100\Omega</math> and <math>10\Omega</math> respectively. Calculate the average voltage, dc output power, ac input power, rectification efficiency and percentage regulation.</p> <p>(ii) Sketch the output Voltage waveform for given circuit</p>  | 10    | CO2 |
| b.    | Draw and Explain the working of tunnel diode & varactor diode with proper diagram and characteristics.   | 10    | CO2 |


## 5. Attempt any one part of the following:

1 x 10 = 10
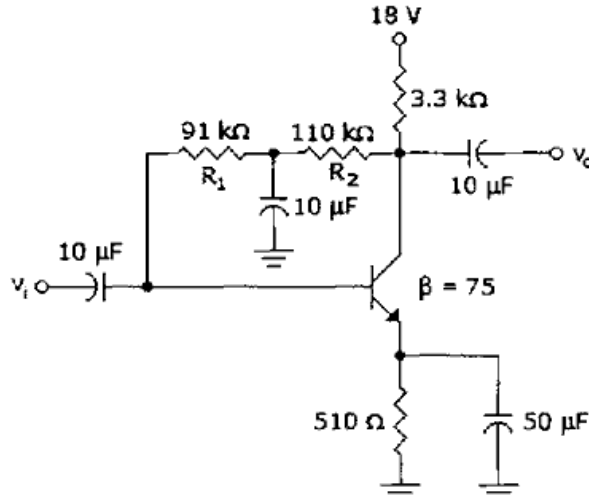
| Q no. | Question   | Marks | CO  |
|-------|--|-------|-----|
| a.    | <p>Calculate the value of <math>V_{CEQ}</math> and <math>I_{CQ}</math> for the given circuit.</p>   | 10    | CO3 |
| b.    | <p>The device parameters for an n-Channel JFET are: Maximum current <math>I_{DSS} = 10\text{mA}</math>, Pinch off voltage, <math>V_p = -4\text{V}</math>. Calculate the drain current for (a) <math>V_{GS} = 0</math> (b) <math>V_{GS} = -1.0\text{V}</math> (c) <math>V_{GS} = -4\text{V}</math>.</p> | 10    | CO3 |

## 6. Attempt any one part of the following:

1 x 10 = 10
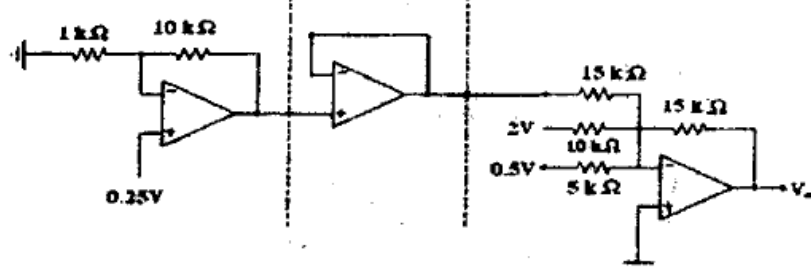
| Q no. | Question  | Marks | CO  |
|-------|---|-------|-----|
| a.    | <p>Find the output of the following Op-Amp Circuit.</p>  <p>Also explain the characteristics of an ideal opamp.</p> | 10    | CO4 |

Paper Id: 199362

Roll No:

|  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

|    |  |    |     |
|----|--|----|-----|
| b. | Define following terms for an Opamp:<br>(i) Slew rate<br>(ii) Virtual ground<br>(iii) CMRR | 10 | CO4 |
|----|--|----|-----|

7. Attempt any *one* part of the following:

1 x 10 = 10

| Q no. | Question  | Marks | CO  |
|-------|---|-------|-----|
| a.    | (i) Explain how we measure voltage, frequency and phase with CRO.<br>(ii) A lissajous pattern on an oscilloscope is stationary. It has 5 vertical tangent values and 6 horizontal tangent values. The frequency of horizontal input is 1800Hz. Determine the frequency of vertical input. | 10    | CO5 |
| b.    | Draw and explain the block diagram of Digital Storage Oscilloscope(DSO) also compare it with analog oscilloscope.   | 10    | CO5 |

<https://www.aktuonline.com>

Whatsapp @ 9300930012

Send your old paper & get 10/-

अपने पुराने पेपर्स भेजे और 10 रुपये पायें,

Paytm or Google Pay से